

Assignment:-2, Unit-2: Graph Theory, Circuit Analysis by Classical Method

- Q1. Determine all the tree and corresponding co-trees for the graph of the network. Then, consider the tree formed by branches (1, 2, 5) using this tree write A , B_f & Q_f .
Fig.1

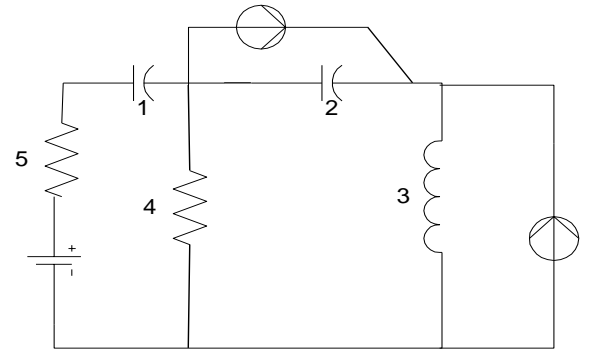


Fig.1

- Q2. Draw the oriented graph of the following matrixes.

$$A = \begin{bmatrix} -1 & 0 & -1 & 1 & 0 & 0 & 1 \\ 0 & -1 & 0 & -1 & 0 & -1 & 0 \\ 1 & 1 & 0 & 0 & -1 & 1 & 0 \end{bmatrix}$$

$$Q_f = \begin{bmatrix} \overbrace{1 \quad 0 \quad 0 \quad 0}^{\text{Twigs}} & \overbrace{-1 \quad 0 \quad 0}^{\text{Links}} \\ 0 & +1 & 0 & 1 \\ 0 & 0 & 1 & 0 \\ 0 & 0 & 0 & 1 \end{bmatrix}$$

- Q3. Draw the graph and find a tree for the network. Consider "O" as a datum node and assuming elements BD and BC as links (R_p & Capacitor), determine the tie-set schedule, branch impedance matrix and source voltage matrix. Obtain the loop equations using the above said matrices. Fig.3

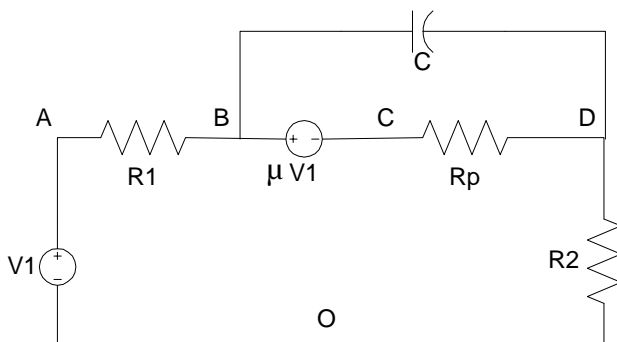


Fig.3

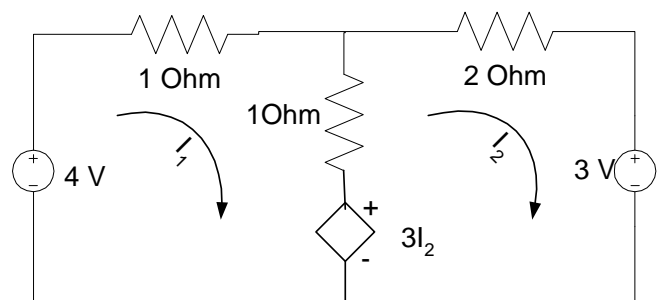


Fig.4

- Q4. Using loop method of analysis, determine currents in all the branches, indicating their directions.
Fig.4 (Ans:-3 A, -1 A, -4 A)

Assignment:-2, Unit-2: Graph Theory, Circuit Analysis by Classical Method

- Q5. Construct a tree in which 10 Ohm and 20 Ohm are tree branches. Using nodal analysis, solve for V_1 & V_2 . Fig.5
(Hint: Assume a resistance parallel with 2 A And a resistance in series with 20 V source
Ans: - $V_1=19.02$ V, $V_2=21.46$ V)

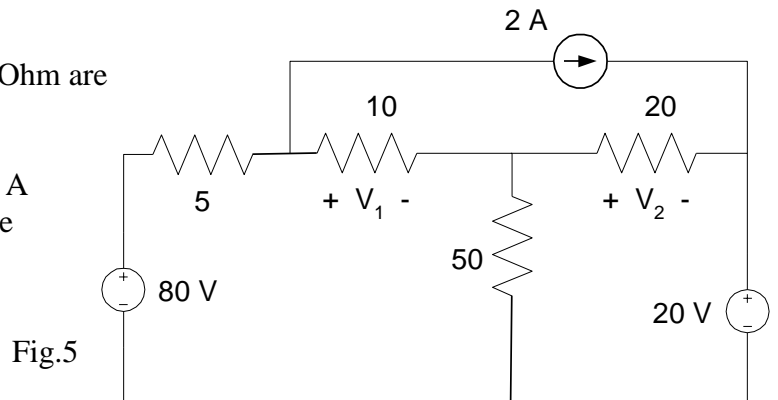


Fig.5

- Q6. Write the node equation for the following network. Fig.6

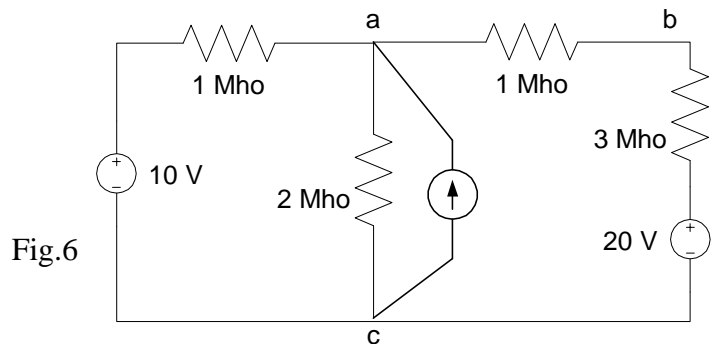


Fig.6

- Q7. Draw the dual of the following networks. Fig.7(a & b)

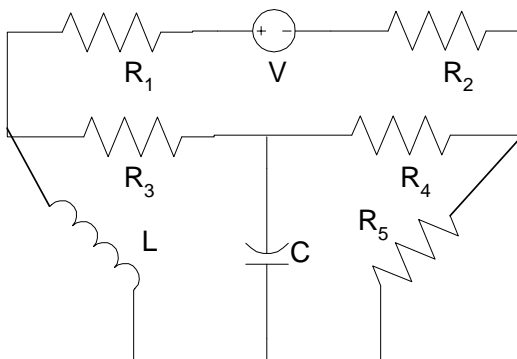


Fig.7.a

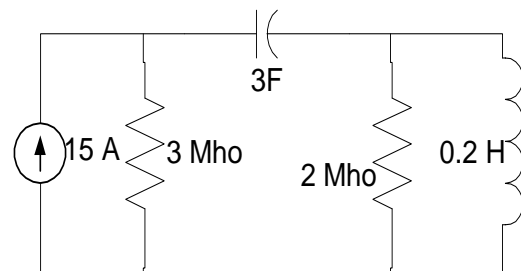


Fig.7.b

- Q8. In the circuit shown in figure 8, switch is closed at $t=0$. Find i_1 , i_2 , $\frac{di_1}{dt}$ & $\frac{di_2}{dt}$ at $t=0^+$.

- Q9. In the circuit shown in figure 9, the switch K is changed from position 1 to position 2 at time $t=0$. Steady state condition having reached before switching. Find out i_1 , $\frac{di_1}{dt}$ & $\frac{di_1^2}{dt}$.

Assignment:-2, Unit-2: Graph Theory, Circuit Analysis by Classical Method

Q10. Figure 10 represents a parallel RLC circuit where $R = 0.1 \text{ Ohm}$, $L = 0.5 \text{ H}$ and $C = 1 \text{ Micro Farad}$. Capacitor has an initial voltage of 10 V , polarity as shown in figure. The switch K is closed at time $t = 0$. Obtain $v(t)$.

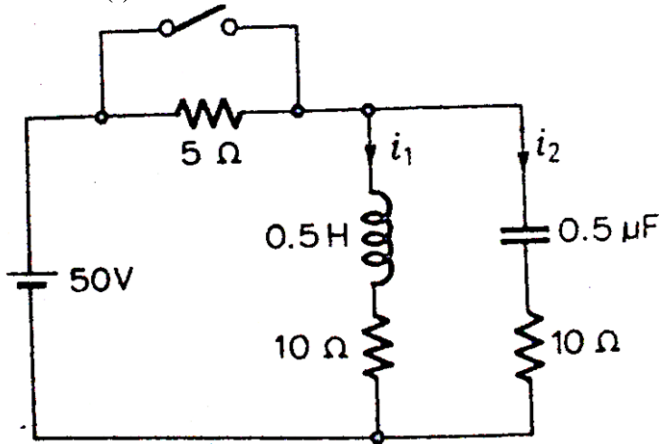


Figure 8

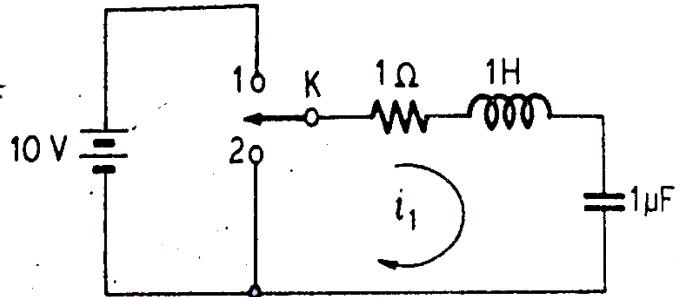


Figure 9

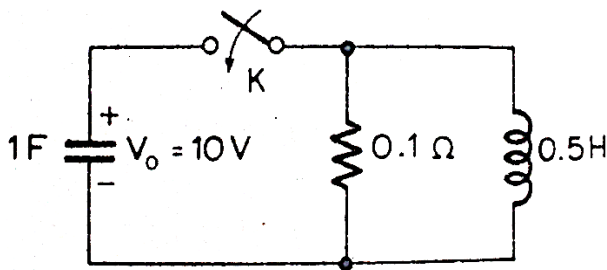


Figure 10