


EXPEREMENT-2

AIM: To verify the Thevenin's Theorem with dc and ac sources using MULTISIM software.

SOFTWARE REQUIRED: MULTISIM software.

THEORY:

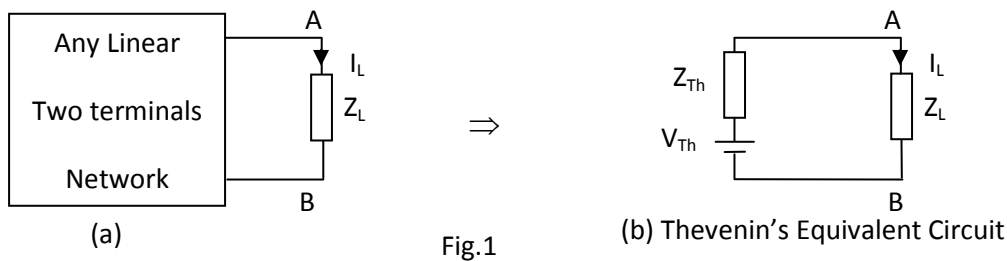Thevenin's theorem: "Any linear two terminal circuits can be replaced by an equivalent network consisting of a voltage source (V_{Th}) in series with impedance Z_{Th} (or R_{Th} for DC network)."



Where


V_{Th} = Open circuit voltage at load terminals

Z_{Th} (or R_{Th}) = Equivalent Impedance (Resistance) of the network at load terminals when the sources are made in-operative.

And
$$I_L = \frac{V_{Th}}{Z_{Th} + Z_L}$$
 Fig.1

Circuits:

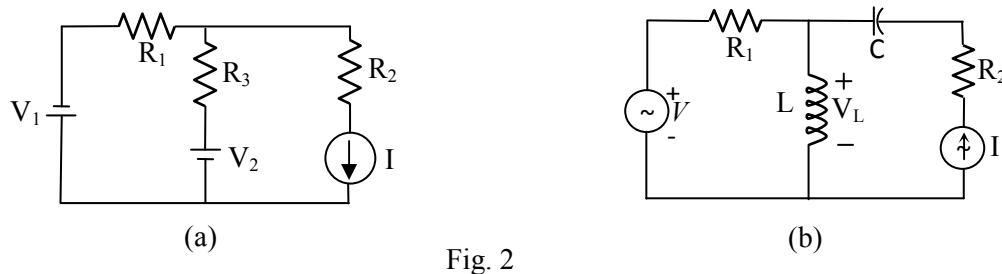- a. For DC source:** Find out current in R_3 in the circuit shown in figure 2a by Thevenin's theorem. Assume any value for V_1 , V_2 , I , R_1 , R_2 but R_3 = your class roll no.



- b. For AC source:** Find out voltage across L in the circuit shown in figure 2b by Thevenin's theorem. Assume any value for V, I, L, C, R₁ but R₂= your class roll no.

SOFTWARE CIRCUITS:

CALCULATIONS:

RESULT: The following circuit verifies the superposition theorem.

PRECAUTION:

1. Ground the circuit before simulation.
2. Design circuit carefully.
3. Save the file properly
4. Don't change the setting the software and computer.