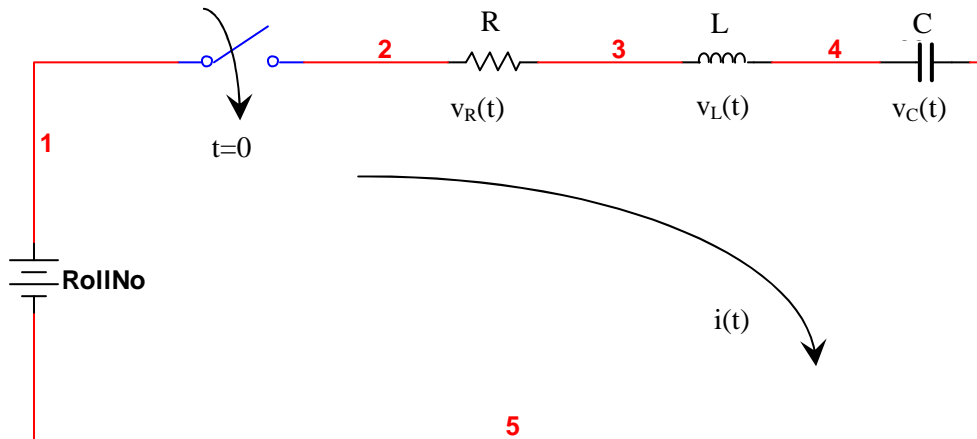


EXPEREMENT-7

AIM: To obtain the transient response of underdamped R-L-C series circuit for step voltage input using MULTISIM software.

SOFTWARE REQUIRED: MULTISIM software.

THEORY: Consider the following series R-L-C circuit. Let the switch is closed at t=0.



When switch is closed at t=0, apply KVL

$$L \frac{di(t)}{dt} + Ri(t) + \frac{1}{C} \int i(t) dt = V \text{ --- (1)}$$

Differentiate and put the values

$$\frac{di^2(t)}{dt^2} + \frac{R}{L} \frac{di(t)}{dt} + \frac{1}{LC} i(t) = 0 \text{ --- (2)}$$

For CF: It's A.E

$$m^2 + \frac{R}{L}m + \frac{1}{LC} = 0$$

$$m_1 \& m_2 = -\frac{R}{2L} \pm \sqrt{\left(\frac{R}{2L}\right)^2 - \frac{1}{LC}}$$

Let

$$\alpha = -\frac{R}{2L} \& \beta = \sqrt{\left(\frac{R}{2L}\right)^2 - \frac{1}{LC}}$$

$$m_1 = \alpha + \beta \& m_2 = \alpha - \beta$$

$$CF = K_1 e^{m_1 t} + K_2 e^{m_2 t}$$

For PI: PI=0

So Complete solution $i(t)=CF+PI$

$$i(t) = K_1 e^{m_1 t} + K_2 e^{m_2 t} \text{ --- (3)}$$

Assuming $\left(\frac{R}{2L}\right)^2 < \frac{1}{LC}$ In this case is imaginary number. Hence roots m_1 & m_2 are complex conjugate. System will become underdamped (or oscillatory).

$$m_1 = \alpha + j\beta, \quad m_2 = \alpha - j\beta$$

If switch is closed at $t=0$

$$i(0^+) = 0 \text{-----(4) put this in equation (3)}$$

$$L \frac{di(0^+)}{dt} + Ri(0^+) + \frac{1}{C} \int i(0^+) dt = V$$

$$L \frac{di(0^+)}{dt} + R \times 0 + 0 = V$$

(at $t = 0^+$, L will be open & C will be shorted)

$$\frac{di(0^+)}{dt} = \frac{V}{L} \frac{A}{Sec} \text{----- (5)}$$

Put condition of equation (4) & (5) in equation (3)


$$K_1 + K_2 = 0 \text{-----(6)}$$

$$\text{And } \frac{V}{L} = K_1 m_1 + K_2 m_2 \text{ --- (7)}$$

Solving equations (6) & (7) $K_1 = -\frac{V}{L(m_2 - m_1)}$ & $K_2 = \frac{V}{L(m_2 - m_1)}$, Putting in equation (3)

$$i(t) = \frac{V}{L(m_2 - m_1)} (-e^{m_1 t} + e^{m_2 t}) \text{ --- (3)}$$

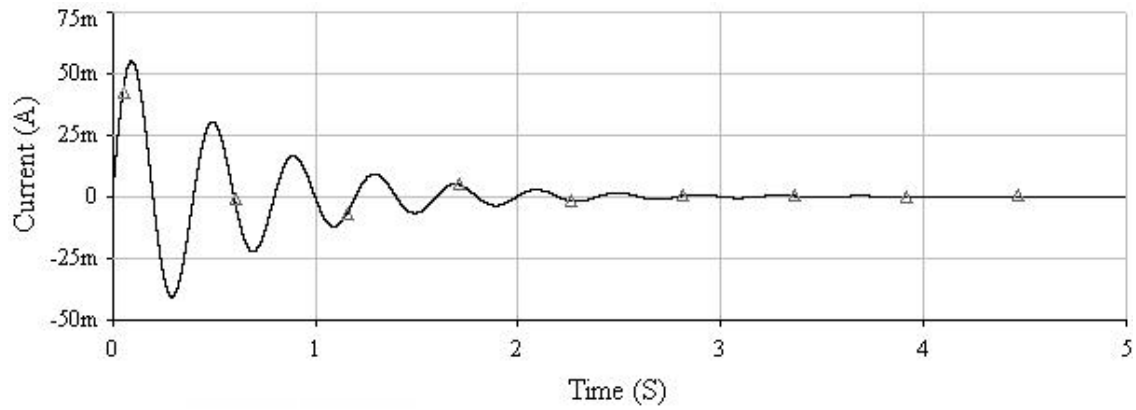
For $V=2$, $R=6$ ohm, $L=2$ H, $C=2$ mF, Trace of $i(t)$ will be as shown bellow



Voltage across R

$$V_R(t) = i(t)R =$$

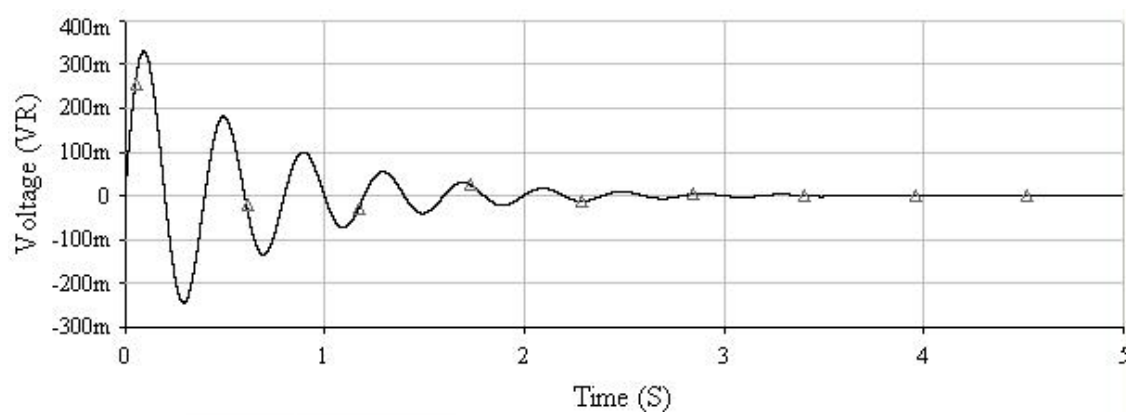
For $V=2$, $R=6$ ohm, $L=2$ H, $C=2$ mF, Trace of $V_R(t)$ will be as shown bellow



Voltage across L

$$V_L(t) = L \frac{di(t)}{dt} =$$

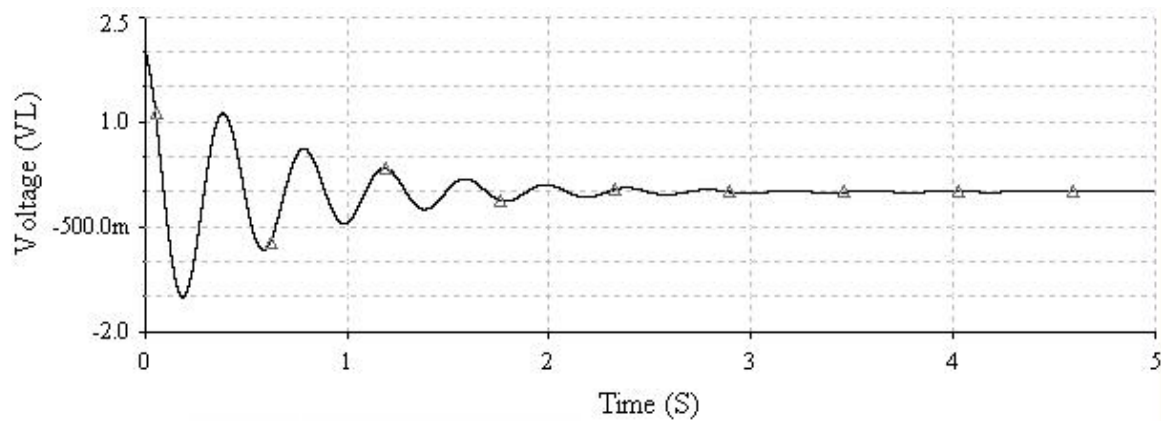
For $V=2$, $R=6$ ohm, $L=2$ H, $C=2$ mF, Trace of $V_L(t)$ will be as shown bellow




Voltage across C

$$V_C(t) = V - V_R(t) - V_L(t) =$$

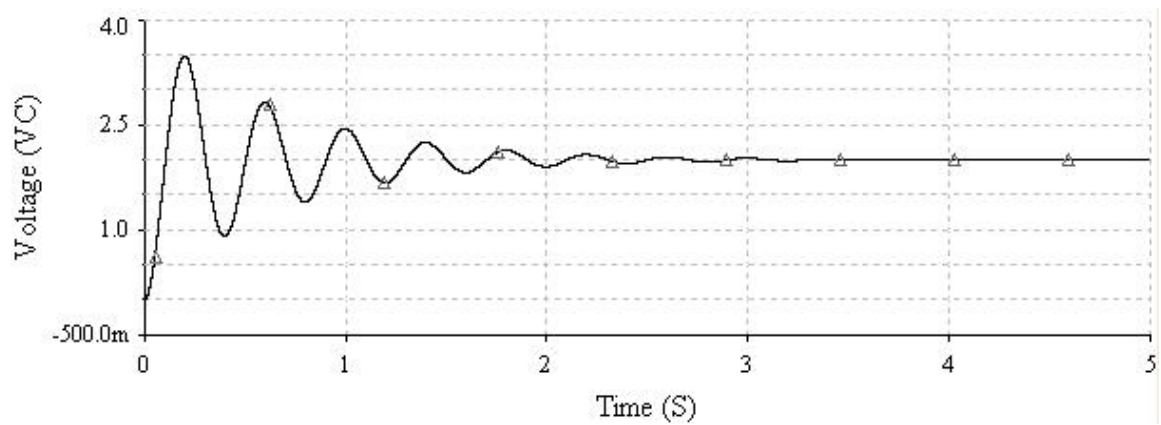For $V=2$, $R=6$ ohm, $L=2$ H, $C=2$ mF, Trace of $V_C(t)$ will be as shown bellow



SOFTWARE CIRCUITS:

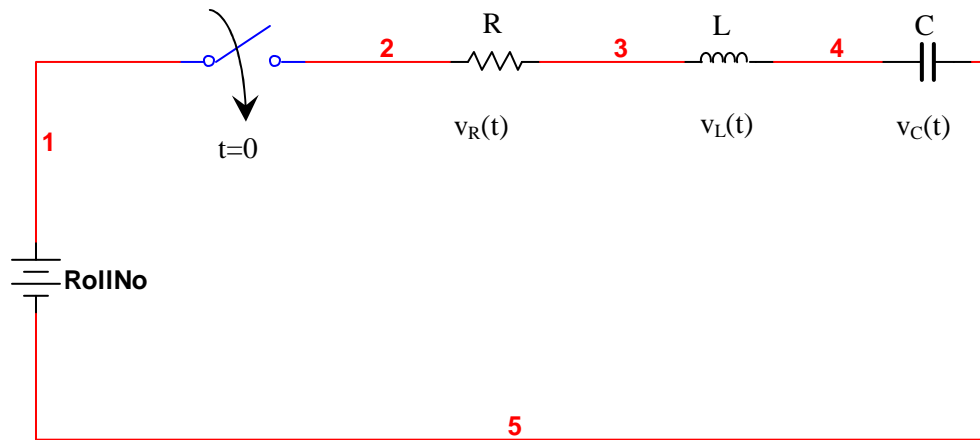

CALCULATIONS: Calculate the expression of $i(t)$, $V_R(t)$, $V_L(t)$ & $V_C(t)$

RESULT:

PRECAUTION And Do's & Don't:

1. Simulation time should be chosen properly.
2. Ground the circuit before simulation.
3. Design circuit carefully.
4. Save the file properly
5. Don't change the setting the software and computer.