	DEHRADUN INSTITUTE OF TECHNOLOGY		LABORATORY MANUAL
	PRACTICAL INSTRUCTION SHEET		
	EXPERIMENT TITLE : OC & SC test on 1-phase transformer		
	EXPERIMENT NO. :	ISSUE NO. :	ISSUE DATE :
REV. NO. V	REV. DATE : 01/01/2016	PAGE /	
DEPTT. : Electrical Engineering	LABORATORY : Intro to Electrical & Electronics Lab EA1210	SEMESTER : I / II	

Objective: - To perform open circuit (OC) & short circuit (SC) test on single phase transformer and calculate the followings.

- Complete parameters of equivalent circuit.
- Efficiency at half of the full load and at unity power factor.

Apparatus Used: - One single phase transformer 2 kVA, 230/230 volts and following apparatus


S.No	Name	Type	Range	Quantity	
1	Single phase autotransformer		15A, 230/0-270 Volts	1	
2	Ammeter	MI	0-1 A	1	For OC test
3	Voltmeter	MI	0-250 V	1	
4	Wattmeter (Low PF 0.2)	Dynamometer	1 A, 250 V	1	
5	Ammeter	MI	0-5 A	1	For SC Test
6	Voltmeter	MI	0-30 V	1	
7	Wattmeter (High PF)	Dynamometer	5 A, 75 V	1	

Theory:

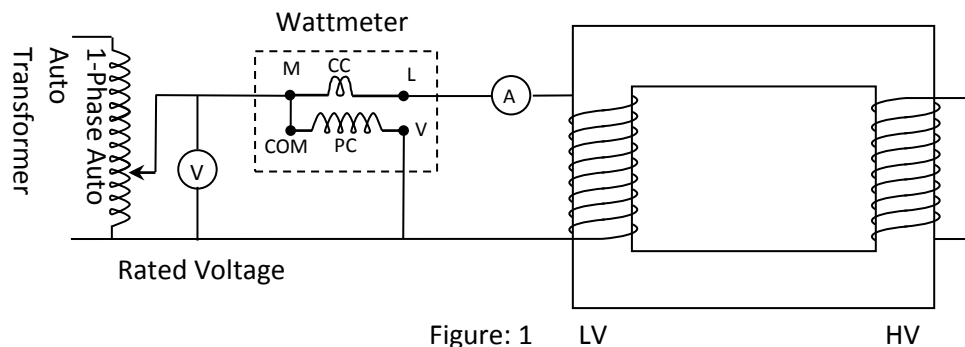
1. Open Circuit (OC) test or No load test:

By OC test we can find out

- Iron losses (P_i)
- No load current (I_0)
- $\cos\phi_0$, I_e , I_m , R_0 & X_0



PREPEARD BY :- Mr. Nafees Ahmed	APPROVED BY :- Dr. Gagan Singh
Visit us at www.eedofdit.weebly.com	

	DEHRADUN INSTITUTE OF TECHNOLOGY		LABORATORY MANUAL
	PRACTICAL INSTRUCTION SHEET		
	EXPERIMENT TITLE : OC & SC test on 1-phase transformer		
	EXPERIMENT NO. :	ISSUE NO. :	ISSUE DATE :
REV. NO. V	REV. DATE : 01/01/2016	PAGE /	
DEPTT. : Electrical Engineering	LABORATORY : Intro to Electrical & Electronics Lab EA1210	SEMESTER : I / II	

Iron losses $P_i =$ Reading of wattmeter (P_0)
 No load current $I_0 =$ Reading of Ammeter
 Let $V =$ Reading of voltmeter
 $P_0 = P_i = VI_0 \cos \phi_0$
 $\Rightarrow \cos \phi_0 = \frac{P_i}{VI_0}$
 $I_e = I_0 \cos \phi_0$
 $I_m = I_0 \sin \phi_0$
 $R_0 = \frac{V}{I_e} \quad \& \quad X_0 = \frac{V}{I_m}$

Note:

- (i) Rated voltage is applied at LV side.
- (ii) This test is generally done on LV side (Why?)

2. Short Circuit (SC) test:

By SC test we can find out

- Copper losses (P_C)
- Equivalent resistance or leakage reactance ($R_{01} \ \& \ X_{01}$ OR $R_{02} \ \& \ X_{02}$) referred to metering side.

Full load Cu losses $P_C =$ Reading of wattmeter (W_{sc})
 Let Short circuit current $I_{sc} =$ Reading of Ammeter
 Short circuit voltage $V_{sc} =$ Reading of voltmeter

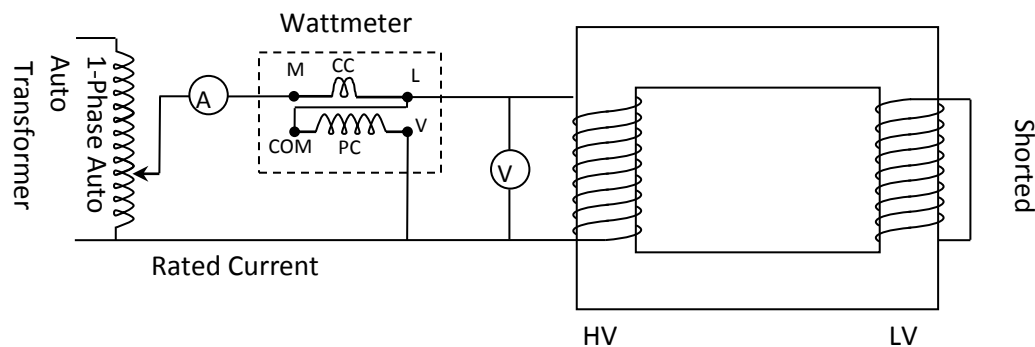



Figure: 2

PREPEARD BY :- Mr. Nafees Ahmed	APPROVED BY :- Dr. Gagan Singh
Visit us at www.eedofdit.weebly.com	

	DEHRADUN INSTITUTE OF TECHNOLOGY		LABORATORY MANUAL
	PRACTICAL INSTRUCTION SHEET		
	EXPERIMENT TITLE : OC & SC test on 1-phase transformer		
	EXPERIMENT NO. :	ISSUE NO. :	ISSUE DATE :
REV. NO. V	REV. DATE : 01/01/2016	PAGE /	
DEPTT. : Electrical Engineering	LABORATORY : Intro to Electrical & Electronics Lab EA1210	SEMESTER : I / II	

$$W_{sc} = I_{sc}^2 R_{eq} \quad (R_{eq} = R_{01} \text{ or } R_{02})$$

$$V_{sc} = I_{sc} Z_{eq} \quad (Z_{eq} = Z_{01} \text{ or } Z_{02})$$

$$X_{eq} = \sqrt{Z_{eq}^2 - R_{eq}^2} \quad (X_{eq} = X_{01} \text{ or } X_{02})$$

Note:

- (i) Rated Current is applied at HV side.
- (ii) This test is generally done on HV side (Why?)
- (iii) Why the position of ammeter and voltmeter is changed as compared to OC test?
- (iv) Why com terminal of wattmeter is connected with terminal L not with terminal M?

3. Efficiency of transformer:

Efficiency at x time of full load

$$\eta = \frac{xP_2}{xP_2 + P_i + x^2P_c} \times 100 \quad \text{Where } P_2 = V_2 I_2 \cos\phi_2 = \text{Rated VA} \times \cos\phi_2$$

$$\cos\phi_2 = \text{Load PF}$$


Circuit Diagram:- See figure 1 & 2

Observation table:-

OC Test			SC Test		
P _i or P ₀ (W)	V (V)	I ₀ (A)	P _c or W _{sc} (W)	V _{sc} (V)	I _{sc} (A)

PREPEARD BY :- Mr. Nafees Ahmed

APPROVED BY :- Dr. Gagan Singh

	DEHRADUN INSTITUTE OF TECHNOLOGY	LABORATORY MANUAL
	PRACTICAL INSTRUCTION SHEET	
	EXPERIMENT TITLE : OC & SC test on 1-phase transformer	
	EXPERIMENT NO. :	ISSUE NO. :
REV. NO. V	REV. DATE : 01/01/2016	PAGE /
DEPTT. : Electrical Engineering	LABORATORY : Intro to Electrical & Electronics Lab EA1210	SEMESTER : I / II

Calculation:-

Equivalent circuit of transformer:

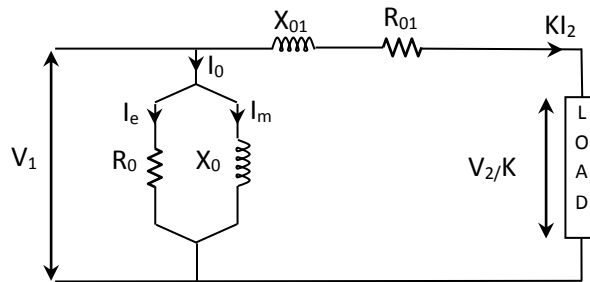


Figure 3: Approximately & simplified Equivalent Circuit Referred to primary side

For OC test: find MF

$$\text{Multiplying Factor (M.F.)} = \frac{VI \cos\Phi}{\text{Full scale deflection(FSD)}} \quad \cos\Phi = 0.2$$

$$\cos\phi_0 = \frac{P_i}{VI_0}$$

$$I_e = I_0 \cos\phi_0$$

$$I_m = I_0 \sin\phi_0$$

$$R_0 = \frac{V}{I_e} \quad \& \quad X_0 = \frac{V}{I_m}$$

For SC test: find MF

$$\text{Multiplying Factor (M.F.)} = \frac{VI \cos\Phi}{\text{Full scale deflection(FSD)}} \quad \cos\Phi = 1$$


$$W_{sc} = I_{sc}^2 R_{eq} \quad (R_{eq} = R_{01} \text{ or } R_{02})$$

$$V_{sc} = I_{sc} Z_{eq} \quad (Z_{eq} = Z_{01} \text{ or } Z_{02})$$

$$X_{eq} = \sqrt{Z_{eq}^2 - R_{eq}^2} \quad (X_{eq} = X_{01} \text{ or } X_{02})$$

PREPEARD BY :- Mr. Nafees Ahmed

APPROVED BY :- Dr. Gagan Singh

	DEHRADUN INSTITUTE OF TECHNOLOGY		LABORATORY MANUAL
	PRACTICAL INSTRUCTION SHEET		
	EXPERIMENT TITLE : OC & SC test on 1-phase transformer		
	EXPERIMENT NO. :	ISSUE NO. :	ISSUE DATE :
REV. NO. V	REV. DATE : 01/01/2016	PAGE /	
DEPTT. : Electrical Engineering	LABORATORY : Intro to Electrical & Electronics Lab EA1210	SEMESTER : I / II	

Efficiency at full load: $x = 1$ & $PF = 1$

$$\eta = \frac{P_2}{P_2 + P_i + P_c} \times 100$$

$$\text{Where } P_2 = V_2 I_2 \cos \phi_2 = \text{Rated VA} \times \cos \phi_2$$

Result: - The OC & SC test has been performed on given transformer and the calculated value of equivalent parameters & efficiency is given in following table

From OC Test					From SC Test			Efficiency (%)
Iron Loss (P_i) (W)	No load Current I_0 (A)	No Load PF $\cos \phi_0$	X_0 (Ω)	R_0 (Ω)	Full load cu loss P_c (W)	R_{eq} (Ω)	X_{eq} (Ω)	

Precautions:-

1. In SC test applied voltage is very less to get the rated short circuit current. Don't give rated voltage otherwise very high current will follow and system will get damage.
2. Make sure that auto transformer is at zero position.
3. The main switch should be at off position before doing the connections.
4. All connection should be tight and clean.
5. The reading in instruments should not exceed from their permissible limit.
6. Don't touch the necked terminals as voltage is high.
7. Always wear shoes when working in the lab. Avoid wearing loose clothes, hanging chains etc.

PREPEARD BY :- Mr. Nafees Ahmed	APPROVED BY :- Dr. Gagan Singh
Visit us at www.eedofdit.weebly.com	