

## Electrical Resonance

Resonance is defined as the condition in a circuit containing at least one inductor and one capacitor when the supply voltage & supply current are in same phase.

At resonance

- i. Angle between V & I is zero
- ii.  $\phi = 0 \Rightarrow \cos \phi = 1$ , Unity power factor
- iii. If Z and Y are given in rectangular form, their imaginary part will be zero i.e.
  - If  $Z = R \pm jX \Rightarrow \text{Im}(Z) = 0 \Rightarrow X = 0$
  - If  $Y = G \pm jB \Rightarrow \text{Im}(Y) = 0 \Rightarrow B = 0$
- iv. If Z and Y are given in polar form, their angle will be zero i.e.
  - If  $Z = |Z| \angle \theta \Rightarrow \theta = 0$
  - If  $Y = |Y| \angle \theta \Rightarrow \theta = 0$

### Types of resonance: Two types

1. **Series Resonance:** Consider the following circuit

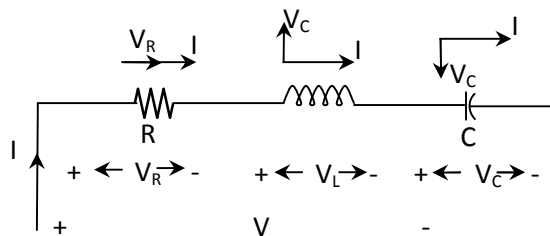


Fig. 1a

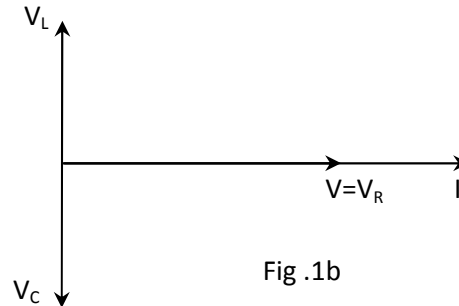


Fig. 1b

$$Z = \sqrt{R^2 + (X_L - X_C)^2}$$

If  $X_L = X_C$  then

- i. Total reactance  $X = X_L - X_C = 0$
- ii. Total impedance  $Z = R = Z_r$  (say)
- iii. Current  $I = \frac{V}{Z} = \frac{V}{R}$  maximum
- iv. Angle between V & I is zero  $\Rightarrow \phi = 0 \Rightarrow \cos \phi = 1$   
This condition is called as series resonance and frequency at which it occurs is called resonance frequency ( $f_r$ ).


So at resonance

$$X_L = X_C \quad \Rightarrow \quad \omega L = 1/\omega C \quad \Rightarrow \quad \omega_r = \frac{1}{\sqrt{LC}} \quad \Rightarrow \quad f_r = \frac{1}{2\pi} \sqrt{\frac{1}{LC}}$$

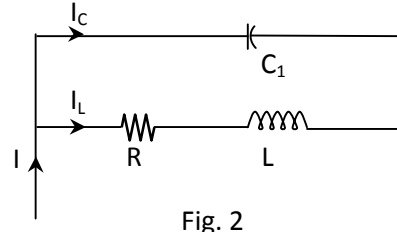2. **Shunt Resonance:** Consider the following parallel circuit

Total admittance

$$\begin{aligned} Y &= Y_1 + Y_2 \\ &= \frac{1}{j\omega C} + \frac{1}{R + j\omega L} \\ &= j\omega C + \frac{(R - j\omega L)}{R^2 + \omega^2 L^2} \\ &= \frac{R}{R^2 + \omega^2 L^2} + j\omega \left( C - \frac{L}{R^2 + \omega^2 L^2} \right) \quad \text{---(1)} \end{aligned}$$



At resonance

$$\text{Im}(Y) = 0 \quad \Rightarrow \quad \left( C - \frac{L}{R^2 + \omega^2 L^2} \right) = 0 \quad \Rightarrow \quad C = \frac{L}{R^2 + \omega^2 L^2}$$

$$\Rightarrow \quad \omega^2 L^2 = \frac{L}{C} - R^2 \quad \text{---(2)}$$

$$\Rightarrow \quad \omega = \sqrt{\frac{1}{LC} - \frac{R^2}{L^2}} \quad \Rightarrow \quad f_r = \frac{1}{2\pi} \sqrt{\frac{1}{LC} - \frac{R^2}{L^2}}$$

$$\text{If } R=0 \Rightarrow \quad f_r = \frac{1}{2\pi} \sqrt{\frac{1}{LC}} \quad \text{same as for series resonance}$$