


Assignment:-1

EA1210-Introduction to EE & ECE-Unit 1: DC N/W Theorems

Note: - All resistances are in ohm (Ω)

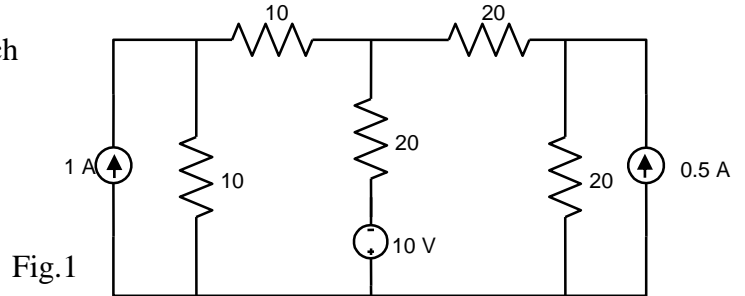Q1. Using Node Analysis, determine current in each branch of the network in fig 1. Also find total power loss in the network..

(Ans: - 0.6 A, 0.3 A, 0.4 A, 0.2 A, 0.6 A, 15 Watts)



Q2. A Wheatstone bridge ABCD has the following details: $AB = 10 \Omega$, $BC = 30 \Omega$, $CD = 15 \Omega$ & $DA = 20 \Omega$. A battery of e.m.f. 2 V and negligible internal resistance is connected between A & C with A positive. A galvanometer of 40 ohm resistance is connected between B & D. Determine the magnitude and direction of current in the galvanometer using Thevenin's theorem.

(Ans: - $R_{Th} = 16.07 \Omega$, $V_{Th} = 0.642 V$, 11.5 mA from B to D)

Q3. Find the current in 10 Ω resistor using (Fig. 2)

- (i) Superposition Theorem
- (ii) Thevenin's Theorem
- (ii) Norton's Theorem

(Ans: - $R_{Th} = 5.35 \Omega$, $V_{Th} = 7 V$, 0.46A)

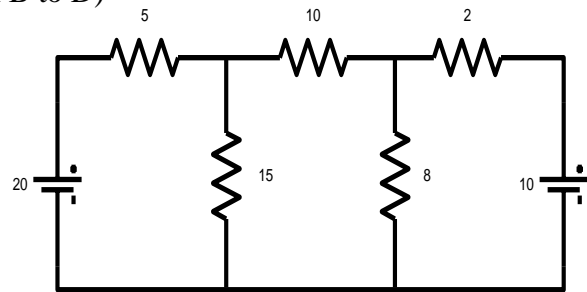


Fig. 2

Q4. Find the current in 3 Ω resistor using (Fig. 3)

- (i) Superposition Theorem
- (ii) Thevenin's Theorem
- (iii) Norton's Theorem

(Ans: - 1 A)

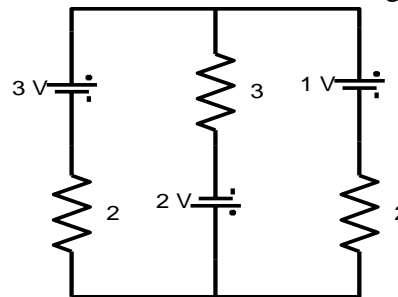


Fig. 3

Q5. Obtain the essential condition for maximum power transfer to the load R_L , and hence determine the maximum power transferred. (Fig.4)

(Ans: - $R_{Th} = R_L = 4.3 \Omega$, $V_{Th} = 10.71 V$, $P_{max} = 26.68 W$)

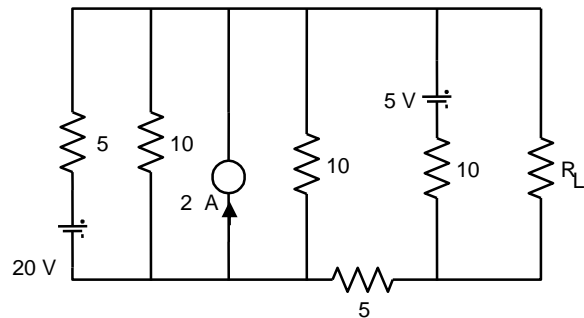


Fig. 4

Assignment:-1


EA1210-Introduction to EE & ECE-Unit 1: DC N/W Theorems

Note: - All resistances are in ohm (Ω)

Q6. Find the current in $2\ \Omega$ connected between A & B resistor using (Fig. 5)

- (i) Superposition Theorem
- (ii) Thevenin's Theorem
- (iii) Norton's Theorem

(Ans: - 1.36 A)

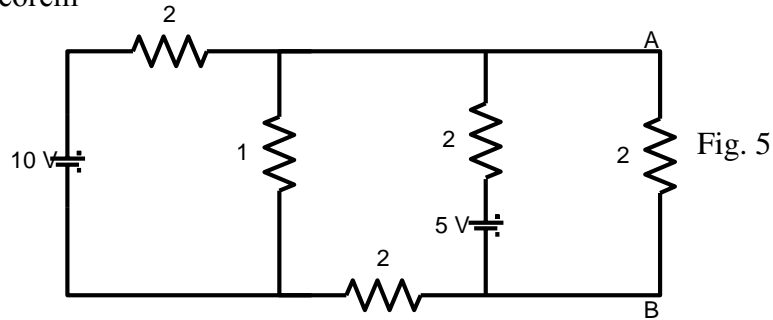

Q7. At P-Q find (fig 6)

- (i) Thevenin's Equivalent circuit
- (ii) Norton's Equivalent circuit

(Ans: - $R_{Th} = 7\ \Omega$, $V_{Th} = 72\ V$, $7\ \Omega$, $I_N = 10.29\ A$)

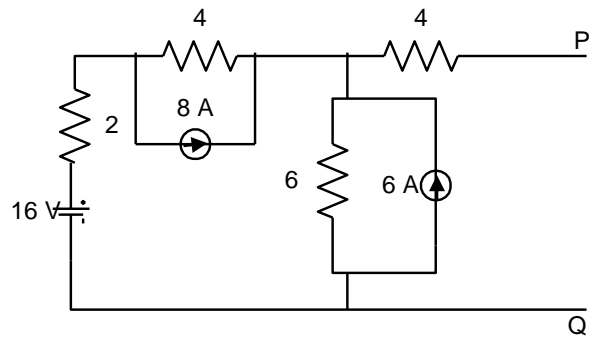


Fig. 6

Q8. At P-Q find (fig 7)

- (i) Thevenin's Equivalent circuit
- (ii) Norton's Equivalent circuit

(Ans: - $R_{Th} = 8.33\ \Omega$, $V_{Th} = 10\ V$,
 $R_N = 8.33\ \Omega$, $I_N = 1.2\ A$)

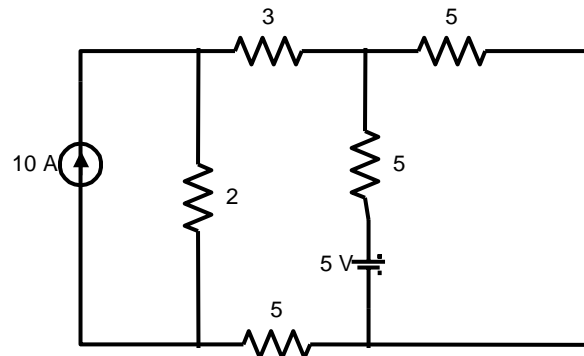



Fig. 7

Assignment:-1


EA1210-Introduction to EE & ECE-Unit 1: DC N/W Theorems

Note: - All resistances are in ohm (Ω)

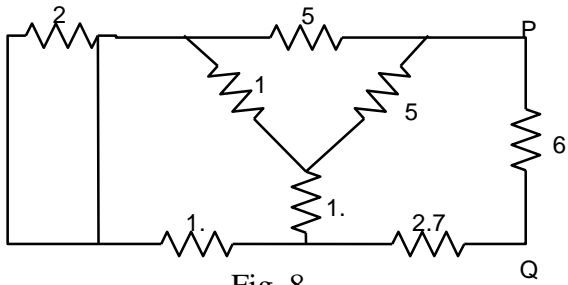Q9. Find resistance between P-Q (fig 8) and A-B (fig 9)



(Ans: - 3Ω)

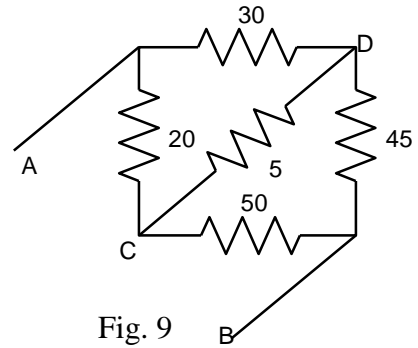

(Ans: - 36Ω)