

Assignment:-2

Note: - All resistances are in ohm (Ω)

- Three Sinusoidal Voltages acting in series are given by $V_1=10 \sin 440t$, $V_2=10\sqrt{2} \sin (440t-45^\circ)$, $V_3=20 \cos 440t$
Determine:-
(i) An expression fro the resultant voltage
(ii) The frequency & rms value of the resultant voltage

Ans:-
 $V=22.36 \sin(440t+26.56^\circ)$
 $f =70 \text{ Hz}$, $V_{\text{rms}}=15.81 \text{ V}$

- Do as directed
(i) Show that the instantaneous power consumed in a pure resistive circuit is not constant but it is fluctuating.
(ii) Show that the Average power consumed by pure L & C is zero.
- Explain the terms
(i) Apparent Power (ii) Active Power (iii) Reactive Power (iv) Power Factor

- Determine (Fig. 1)
(i) The current & power consumed in each branch.
(ii) The supply current & power factor.

Ans:-
 $I_1=10 \angle 45^\circ$ $I_2=10 \angle -15^\circ$ $I_3=10 \angle 05^\circ$
1000 W, 500 W, 500 W,
 $I=20 \angle 45^\circ$, P.F.=1.0

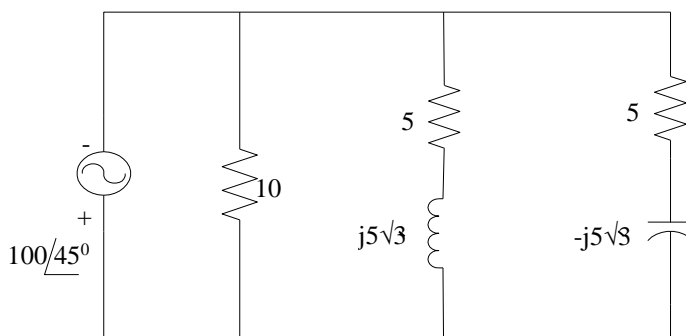


Fig. 1

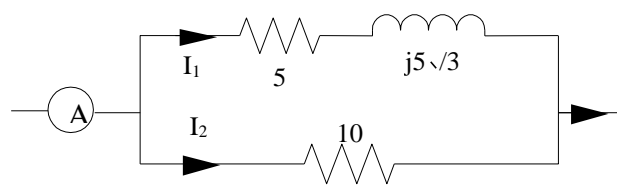


Fig. 2

- Total power consumed by both branches of the circuit shown in Fig. 2 is 2200 W. Calculate the power of each breach and the reading of the ammeter.

Ans:-
 $P_1=1200 \text{ W}$, $P_2=1000 \text{ W}$, $I=19.23 \text{ A}$

- In the series parallel circuit of Fig. 3 the parallel branches A & B are in series with C. The impedance are $Z_A= (4+j3) \Omega$, $Z_B= (10-j7) \Omega$ & $Z_C= (6+j5) \Omega$. If the voltage applied to the circuit is 200 V at 50 Hz, calculate
(i) Current I_A , I_B & I_C .
(ii) The total power factor for the whole circuit. Draw vector diagram also.

Assignment:-2

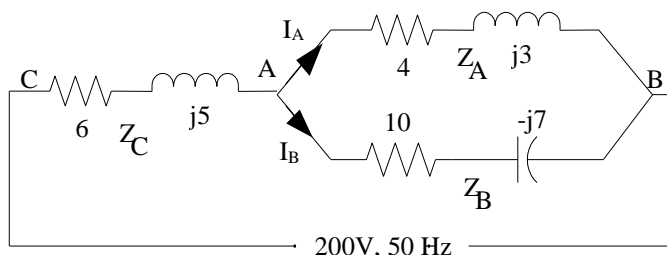


Fig. 3

Ans:-

$$I_A = 14.2 \angle 51.25^\circ \text{ A}, I_B = 5.82 \angle 20.65^\circ \text{ A},$$

$$I_C = 16.95 \angle -32.2^\circ \text{ A}, \text{P.F} = 0.846 \text{ lagging}$$

7. Three identical coils connected in delta across 400 V, 50 Hz, 3- phase ac supply, take a line current of 17.32 A at power factor of 0.8 lagging. Calculate (i) The phase current (ii) the resistance and inductance of each coil (iii) the power drawn by each coil. (Ans: $I_p=10 \text{ A}$, $R_p=32$, $L=76.4 \text{ mH}$, $P= 3200 \text{ Watt}$)
8. With the aid of a phasor diagram show that the power and power factor of a balanced 3-phase load can be measured by two wattmeters.
9. For a certain load, one of the wattmeter reads 20 kW and the other 5 kW. Calculate the power and power factor of the load when (i) both wattmeters read positive value (ii) one wattmeter reads negative value. (Ans.:-25 KW, 0.6933, 15 KW, 0.3273).
10. A 3-phase 500 V motor has 0.4 power factor lagging. Two wattmeters are connected to measure the input, they show the total input to be 30 kW. Find the reading of each wattmeter. (Ans: - 34.843 & - 4.843 Watts)
11. Explain the single line diagram of power system.
12. Explain the principle of operation of a single phase transformer. What are the types of transformers?