

Transistor Biasing

Nafees Ahamad

Asstt. Prof., EECE Deptt, DIT University, Dehradun

Website: www.eedofdit.weebly.com

Introduction

- ▶ The basic function of transistor is to do amplification. (CE connection)
- ▶ *We should have faithful Amplification.* (change in amplitude but not in shape)
- ▶ For this
- ▶ Input circuit (*i.e.* B-E junction) of the transistor always remains forward biased*
- ▶ output circuit (*i.e.* C-B junction) always remains always reverse biased*

*Irrespective of input signal

Faithful Amplification

▶ *Raising the strength of a weak signal without any change in its shape: Faithful Amplification*

▶ for achieving faithful amplification, following basic conditions must be satisfied :

▶ (i) **Proper** zero signal collector current

▶ (ii) **Minimum proper** base-emitter voltage (V_{BE}) at any instant ($V_{BE} > 0.5V$ for Ge & $> 0.7V$ for Si transistor)

▶ (iii) **Minimum proper** collector-emitter voltage (V_{CE}) at any instant ($V_{CE} > 0.5V$ for Ge & $> 1V$ for Si transistor)

To ensure I/p ckt is always forward biased

To ensure O/p ckt is always reverse biased

Fulfilment of these conditions is known as transistor biasing.

Transistor Biasing

- ▶ Fulfilment of above conditions is known as transistor biasing.


Question on Transistor Biasing

- ▶ *Q1. An npn silicon transistor has $V_{CC} = 6\text{ V}$ and the collector load $R_C = 2.5\text{ k}\Omega$. Find :*
- ▶ *(i) The maximum collector current that can be allowed during the application of signal for faithful amplification.*
- ▶ *(ii) The minimum zero signal collector current required.*

Question on Transistor Biasing...

- ▶ **Solution:**
- ▶ **(i)** We know that for faithful amplification, V_{CE} should not be less than 1V for silicon transistor.
- ▶ \therefore Max. voltage allowed across $R_C = 6 - 1 = 5 \text{ V}$
- ▶ \therefore Max. allowed collector current = $5 \text{ V}/R_C = 5 \text{ V}/2.5 \text{ k}\Omega = 2 \text{ mA}$
- ▶ Thus, the maximum collector current allowed during any part of the signal is 2 mA.
- ▶ If the collector current is allowed to rise above this value, V_{CE} will fall below 1 V.


Question on Transistor Biasing...

 

Question on Transistor Biasing...

- ▶ *(ii)* During the negative peak of the signal, collector current can at the most be allowed to become zero.
(see figure on next slide)
- ▶ As the negative and positive half cycles of the signal are equal, therefore, the change in collector current due to these will also be equal but in opposite direction.
- ▶ \therefore Minimum zero signal collector current required = $2 \text{ mA}/2$
= **1 mA**

Question on Transistor Biasing...

 

Question on Transistor Biasing...

- ▶ During the positive peak of the signal (Point A in above figure)
- ▶ $i_C = 1 + 1 = 2\text{mA}$
- ▶ During the negative peak (point B in above figure),
- ▶ $i_C = 1 - 1 = 0\text{ mA}$

Inherent Variations of Transistor Parameters

- ▶ In practice, the transistor parameters such as β , V_{BE} are not the same for every transistor even of the same type.
- ▶ The major reason for these variations is that transistor is a new device and manufacturing techniques have not too much advanced.
- ▶ The inherent variations of transistor parameters may change the operating point, resulting in unfaithful amplification.
- ▶ So the operating point should be independent of transistor parameters variations.

Stabilisation

- ▶ The collector current in a transistor changes rapidly when
- ▶ *(i)* the temperature changes,
- ▶ *(ii)* the transistor is replaced by another of the same type. This is due to the inherent variations of transistor parameters.
- ▶ Due to above the operating point (*i.e.* zero signal I_C and V_{CE}) also changes.
- ▶ Stabilisation means to keep the operating point fixed *i.e.* independent of above changes

Stabilisation...

- ▶ **Need for Stabilisation:** Stabilisation of the operating point is necessary due to the following reasons :
- ▶ **(i) Temperature dependence of I_C :** The collector leakage current I_{CBO} is greatly depends on temperature, so I_C .
- ▶ **(ii) Individual variations:** parameters of any two transistor are not same.
- ▶ **(iii) Thermal runaway:** I_{CBO} keeps on increasing due to temp rise if operating point is not fixed, which result in thermal runaway of transistor.

Essentials of a Transistor Biasing Circuit

- ▶ The biasing network should meet the following requirements
 - ▶ (i) It should ensure proper zero signal collector current.
 - ▶ **(ii)** It should ensure that V_{CE} does not fall below 0.5 V for Ge transistors and 1 V for silicon transistors at any instant.
 - ▶ **(iii)** It should ensure the stabilisation of operating point.

Stability Factor

- ▶ The rate of change of collector current I_C w.r.t. the collector leakage current I_{CBO} (I_{CO}) at constant β and I_B is called stability factor(S)

$$S = \frac{dI_C}{dI_{CO}} \text{ at constant } I_B \text{ and } \beta$$

- ▶ “S” should be as low as possible (ideally 1, practically <25)

Stability Factor...

- ▶ For C.E. configuration


$$S = \frac{\beta + 1}{1 - \beta \left(\frac{dI_B}{dI_C} \right)}$$

Methods of Transistor Biasing

- ▶ For simplicity and economy reason, single battery can be used for biasing of both i/p and o/p circuits
- ▶ The following are the most commonly used methods of obtaining transistor biasing from one source of supply (*i.e.* V_{CC}):
 - ▶ *(i)* Base resistor method (fixed Bias)
 - ▶ *(ii)* Emitter bias method
 - ▶ *(iii)* Biasing with collector-feedback resistor
 - ▶ *(iv)* Voltage-divider bias

Base resistor method

 - ▶ A high resistance R_B (several hundred $k\Omega$) is connected between the base and +ve end of supply for *npn* and between base and -ve end supply for *pnp* transistor.



For pnp transistor

Base resistor method...

- ▶ **Circuit analysis:** Find the value of R_B so that required collector current flows in the zero signal conditions.
- ▶ Let I_C be the required zero signal collector current.

$$\therefore I_B = \frac{I_C}{\beta}$$

- ▶ Considering the closed circuit *ABENA* and applying KVL, we get,

$$V_{CC} = I_B R_B + V_{BE}$$

$$\Rightarrow R_B = \frac{V_{CC} - V_{BE}}{I_B}$$

V_{BE} is very small so may be neglected sometimes

Base resistor method...

- ▶ Stability factor:

$$S = \frac{\beta + 1}{1 - \beta \left(\frac{dI_B}{dI_C} \right)}$$

- ▶ In fixed-bias method of biasing, I_B is independent of I_C so that $dI_B/dI_C = 0$.
- ▶ So $S = \beta + 1$

Base resistor method...


- ▶ **Advantages:**
- ▶ **(i)** This biasing circuit is very simple as only one resistance R_B is required.
- ▶ **(ii)** Biasing conditions can easily be set and the calculations are simple.
- ▶ **(iii)** There is no loading of the source by the biasing circuit since no resistor is employed across base-emitter junction.

Base resistor method...

- ▶ **Disadvantages :**
- ▶ *(i)* This method provides poor stabilisation.
- ▶ *(ii)* The stability factor is very high (chances of thermal runaway.)

Base resistor method...

 
- Q1. Figure shows that a silicon transistor with $\beta = 100$ is biased by base resistor method. Draw the d.c. load line and determine the operating point. What is the stability factor?



Base resistor method...

- ▶ **Solution:** $V_{CC} = 6\text{ V}$, $R_B = 530\text{ k}\Omega$, $R_C = 2\text{ k}\Omega$
- ▶ **D.C. load line:**
- ▶ From above diagram $V_{CE} = V_{CC} - I_C R_C$ ---(1)
- ▶ Put $I_C = 0$ in equ(1)
- ▶ $V_{CE} = V_{CC} - I_C R_C \quad \Rightarrow \quad V_{CE} = V_{CC} = 6\text{ V}$ *Point B*
- ▶ Put $V_{CE} = 0$ in equ(1)
- ▶ $0 = V_{CC} - I_C R_C \quad \Rightarrow \quad I_C = V_{CC} / R_C = 6 / 2\text{ k}\Omega = 3\text{ mA}$ *Point A*
- ▶ *Now draw the dc load line joining points A & B (Next Slide)*

Base resistor method...

 

Base resistor method...

- ▶ **Operating point Q:**
- ▶ As it is a silicon transistor, therefore, $V_{BE} = 0.7V$
- ▶ Apply KVL at i/p circuit

$$V_{CC} = I_B R_B + V_{BE}$$

$$I_B = \frac{V_{CC} - V_{BE}}{R_B} = \frac{(6 - 0.7) \text{ V}}{530 \text{ k}\Omega} = 10 \mu\text{A}$$

$$I_C = \beta I_B = 100 \times 10 = 1000 \mu\text{A} = 1 \text{ mA}$$

Base resistor method...

$$V_{CE} = V_{CC} - I_C R_C = 6 - 1 \text{ mA} \times 2 \text{ k}\Omega = 6 - 2 = 4 \text{ V}$$

\therefore Operating point is **4 V, 1 mA.**

- ▶ Operating point (Q) is shown on dc load line
- ▶ Stability Factor:


$$S = \beta + 1 = 100 + 1 = \mathbf{101}$$

Emitter Bias Circuit



Biasing with Collector Feedback Resistor

 - ▶ In this method, one end of R_B is connected to the base and the other end to the collector as shown in figure



Biasing with Collector Feedback Resistor...

- ▶ **Circuit analysis:**
- ▶ The required value of R_B needed to give the zero signal current I_C can be determined as follows
- ▶ $V_{CC} = (I_C + I_B) R_C + I_B R_B + V_{BE} \approx (I_C) R_C + I_B R_B + V_{BE}$
[As $I_C \gg I_B$ so neglecting]

$$\begin{aligned} \Rightarrow R_B &= \frac{V_{CC} - V_{BE} - I_C R_C}{I_B} \\ &= \frac{V_{CC} - V_{BE} - \beta I_B R_C}{I_B} \quad (\because I_C = \beta I_B) \end{aligned}$$

Biassing with Collector Feedback Resistor...

- ▶ Stability factor: $S < (\beta + 1)$

Biassing with Collector Feedback Resistor...

- ▶ **Advantages:**


- ▶ *(i)* It is a simple method as it requires only one resistance R_B .
- ▶ *(ii)* This circuit provides some stabilisation of the operating point.

- ▶ **Disadvantages:**

- ▶ *(i)* The circuit does not provide good stabilisation.
- ▶ *(ii)* This circuit provides a negative feedback which reduces the gain of the amplifier.

Biasing with Collector Feedback Resistor...

 
- Q: Figure shows a silicon transistor biased by collector feedback resistor method. Determine the operating point. Given that $\beta = 100$.



Ans Operating point is **10.4 V, 9.6 mA.**

Voltage Divider Bias Method

 - ▶ This is the most widely used method.
- ▶ In this method, two resistances R_1 and R_2 are connected across the supply voltage V_{CC} .



Voltage Divider Bias Method...

► Circuit analysis:

► (i) Collector current I_C :

$$I_1 = \frac{V_{CC}}{R_1 + R_2} \Rightarrow \text{Voltage across } R_2, V_2 = \left(\frac{V_{CC}}{R_1 + R_2} \right) R_2$$

► Apply KVL to base circuit

$$V_2 = V_{BE} + V_E \Rightarrow V_2 = V_{BE} + I_E R_E \Rightarrow I_E = \frac{V_2 - V_{BE}}{R_E}$$

$$I_C = \frac{V_2 - V_{BE}}{R_E} \quad \text{Since } I_E \approx I_C$$

Voltage Divider Bias Method...

- ▶ **(ii) Collector-emitter voltage V_{CE}**
- ▶ Applying KVL to the collector side
- ▶ $V_{CC} = I_C R_C + V_{CE} + I_E R_E$
- ▶ $= I_C R_C + V_{CE} + I_C R_E$ (as $I_E \approx I_C$)
- ▶ $= I_C (R_C + R_E) + V_{CE}$
- ▶ $\therefore V_{CE} = V_{CC} - I_C (R_C + R_E)$

Voltage Divider Bias Method...

- Stability factor:

$$S = \frac{(\beta + 1)(R_0 + R_E)}{R_0 + R_E + \beta R_E}$$

$$\text{where } R_0 = \frac{R_1 R_2}{R_1 + R_2}$$


$$= (\beta + 1) \times \frac{1 + \frac{R_0}{R_E}}{\beta + 1 + \frac{R_0}{R_E}}$$

- If the ratio R_0/R_E is very small, then R_0/R_E can be neglected as compared to 1 So

$$S = (\beta + 1) \times \frac{1}{\beta + 1} = 1$$

Voltage Divider Bias Method...

 - Q. Figure shows the voltage divider bias method. Draw the d.c. load line and determine the operating point. Assume the transistor to be of silicon.



Voltage Divider Bias Method...

- ▶ **Solution:**
- ▶ **d.c. load line:**
- ▶ The collector-emitter voltage V_{CE} is given by :
- ▶ $V_{CE} = V_{CC} - I_C (R_C + R_E)$
- ▶ Put $I_C = 0$ in above equ $\Rightarrow V_{CE} = V_{CC} = 15\text{ V}$ *point B*
- ▶ Put $V_{CE} = 0$ in above equ $\Rightarrow I_C = V_{CC} / (R_C + R_E) = 15 / (1 + 2) \text{K } \Omega = 15\text{ mA}$ *Point A*
- ▶ By joining points A and B, the d.c. load line AB is constructed


Voltage Divider Bias Method...

- ▶ Operating point:
- ▶ For Si transistor $V_{BE} = 0.7 \text{ V}$
- ▶ Voltage across $5 \text{ k}\Omega$ is

$$V_2 = \frac{V_{CC}}{10 + 5} \times 5 = \frac{15 \times 5}{10 + 5} = 5 \text{ V}$$

$$I_E = \frac{V_2 - V_{BE}}{R_E} = \frac{5 - 0.7}{2 \text{ k}\Omega} = \frac{4.3 \text{ V}}{2 \text{ k}\Omega} = 2.15 \text{ mA}$$

$$I_C \approx I_E = 2.15 \text{ mA}$$

 

Voltage Divider Bias Method...

► Again

► $V_{CE} = V_{CC} - I_C (R_C + R_E)$ Put $I_C = 2.15 \text{ mA}$

$$\begin{aligned} V_{CE} &= V_{CC} - I_C (R_C + R_E) \\ &= 15 - 2.15 \text{ mA} \times 3 \text{ k}\Omega = 15 - 6.45 = 8.55 \text{ V} \end{aligned}$$

∴ Operating point is **8.55 V, 2.15 mA.**

► Operating point (Q) is shown on dc load line

Thank you